

RT Box

DEMO MODEL

Three-level Grid-connected NPC Solar Inverter with LCL-filter and Active Damping

Last updated in RT Box Target Support Package 2.1.7

www.plexim.com

- ▶ Request a PLECS and PLECS Coder trial license
- ▶ Get the latest RT Box Target Support Package
- ▶ Check the PLECS and RT Box documentation

1 Overview

This RT Box demo model features a grid-connected three-level neutral-point clamped (NPC) inverter with closed-loop control using a space-vector pulse-width modulation (SVPWM) scheme. This demo model has the following features:

- The plant and controller models are implemented in separate subsystems. This allows a complete transient offline simulation in PLECS, as well as a real-time simulation of both controller and plant model. In the real-time setup the plant model is deployed on an RT Box together with either another RT Box as the controller or by using a dedicated and already programmed microcontroller.
- The inverter delivers 50 kW from an 800 V DC input to a 50 Hz, 230 V_{rms} stiff grid. The link between the inverter and the stiff grid features an LCL-filter. The resonance brought by the LCL-filter may lead to controller instability, thus some damping technique is needed to suppress this resonance peak. In this demo model, an active damping technique is employed over passive damping, with the merit of less power losses.

This document describes the implementation of the power stage and controls using the PLECS Electrical and Control domains. It presents the current control and modulation with a special focus on the three-level SVPWM technique, and the necessary neutral-point balancing algorithm is also included.

The execution time represents the actual time it takes to execute one calculation step of the PLECS model on the RT Box hardware. The chosen discretization step sizes and average execution times for each subsystem in this demo model are shown in Fig. 1.

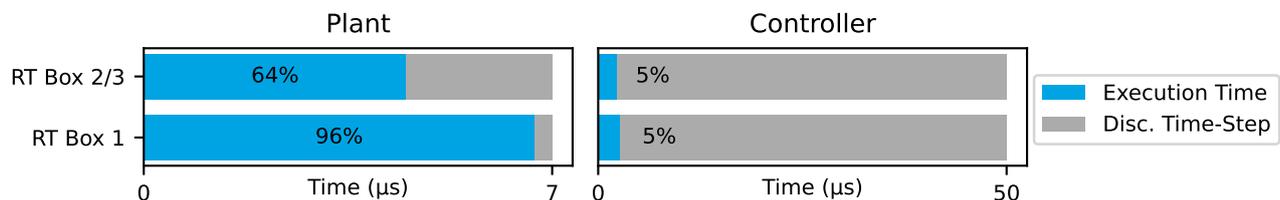


Figure 1: Performance overview for the execution on two RT Boxes

1.1 Requirements

To run this demo model, the following items are needed (available at www.plexim.com):

- Two PLECS RT Boxes and one PLECS Coder license
- The RT Box Target Support Package
- Follow the step-by-step instructions on configuring PLECS and the RT Box in the Quick Start guide of the RT Box User Manual.
- Two 37 pin Sub-D cables to connect the boxes front-to-front.

Note that this demo model is targeted at two RT Boxes application, with one running the Plant and the other running the Controller. In this way, the execution time of each real-time target is minimized. Besides, the setup can easily transition to a HIL or RCP test later on.

However if the user has only one RT Box available, please check the corresponding models targeted for one RT Box application. In this case, two 37 pin Sub-D cables are still needed to connect in front Analog Out interface with Analog In interface, and Digital Out interface with Digital In interface.

- For RT Box 2 and 3, by default the multi-tasking feature is enabled in this demo. “Controller” part is circled with a Task frame block, and runs in one core. The rest of the circuit on the schematic belongs to the “Base task”, and runs in another core. In this way the computational effort is split onto different cores. Please check the default setting under **Scheduling** tab of the **Coder options...** window.

- For RT Box 1, single-tasking should be used which runs both the Plant and the Controller on the same one core of the RT Box 1.

Note This model contains model initialization commands that are accessible from:

PLECS Standalone: The menu **Simulation + Simulation Parameters... + Initializations**

PLECS Blockset: Right click in the **Simulink model window + Model Properties + Callbacks + InitFcn***

2 Model

The top level schematic of the demo model is depicted in Fig. 2, and it is split into two subsystems: “Plant” and “Controller”. To run each subsystem on an RT Box, the subsystems have to be configured as **atomic units** and enabled for **code generation** by right-clicking on the subsystem and choosing **Subsystem + Execution settings...**

A Delay block (z^{-1}) with a sample time equal to one controller discretization step is added to the of-line simulation before the analog input of the controller subsystem. This emulates the calculation time delay of one control step in the real-time application.

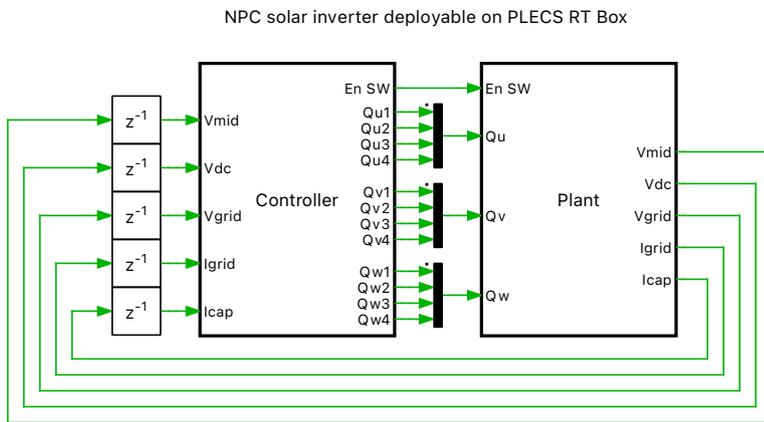


Figure 2: Top level schematic of the controller and three-level NPC inverter plant model

2.1 Three-Level NPC Inverter with LCL-Filter and Active Damping

Fig. 3 shows the circuit model on the “Plant” side, which comprises a three-level NPC inverter connected to the grid through an LCL-filter.

- **DC input:** The DC input is modeled with a simplified photovoltaic (PV) panel model. The block input is the relative solar intensity level (nominal value of 1) set by the Constant block “Sun”. The PV panel output is the intensity level multiplied with a fixed DC voltage of 800 V.
- **Upper and lower half DC capacitors:** The upper and lower half DC capacitors have the same 1.1 mF capacitance value, however, in order to see the effect of the neutral-point balancing algorithm, different initial voltage values are set. Later in the real-time simulation result in section 3, one can see that the upper and lower half DC capacitors, with initial voltages of 450 V and 350 V, respectively, settle at a balanced 400 V and 400 V. The neutral-point balancing algorithm is further discussed in section 2.2.

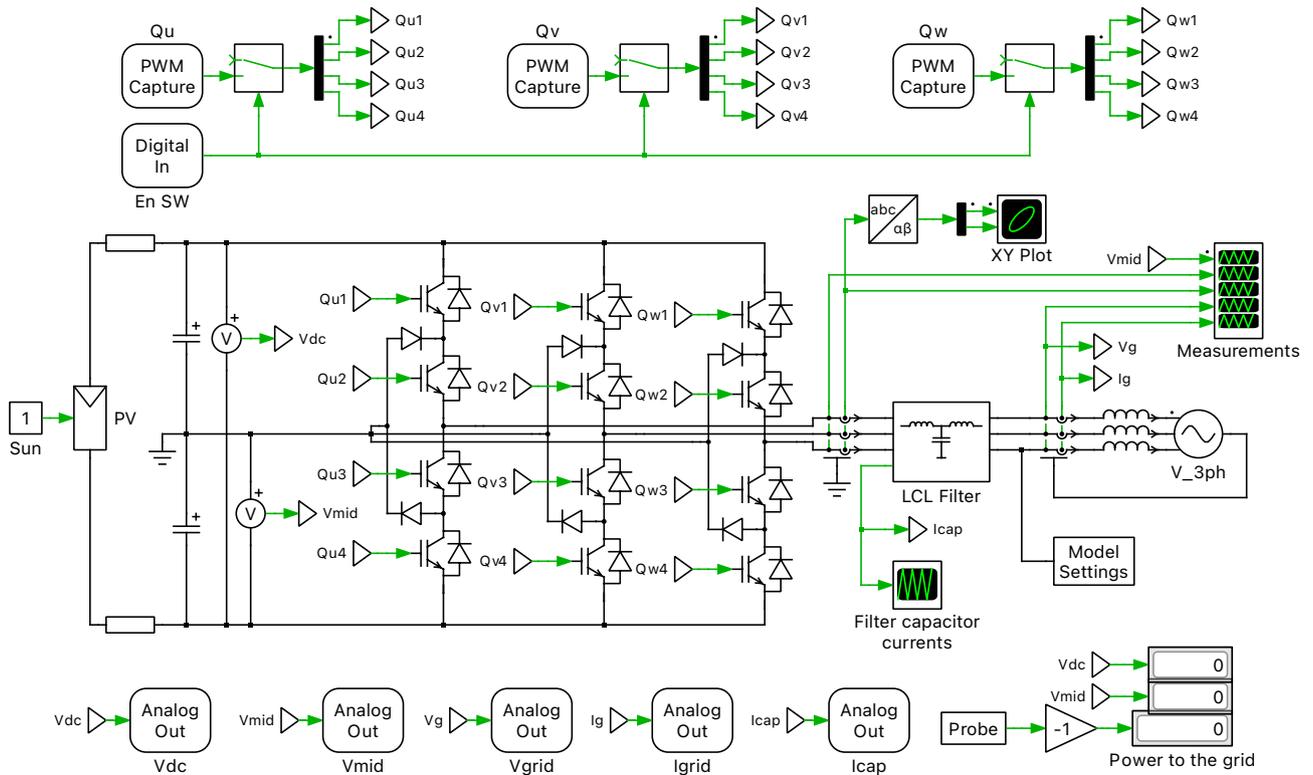


Figure 3: Schematic of the grid-connected three-level NPC inverter with LCL-filter and active damping

- Three-level NPC inverter:** The IGBT 3-Level Half Bridge power modules from the PLECS component library are used to build up the NPC inverter topology. The modules use the sub-cycle average configuration together with the PWM Capture blocks. This ensures that incoming switching signals are sampled with high resolution, and subsequently physical states are properly calculated. This configuration is able to run online in real-time, as well as offline with a variable-step solver.

The plant model uses different blocks from the RT Box Target Support Library to access the physical input and output ports of the RT Box: the PWM Capture and Analog Output blocks, respectively. A generic description of these blocks is given in the RT Box Target Support package documentation or the “Boost Converter” RT Box demo model.

LCL-filter design

Due to the pulsating voltage at the three-level inverter output nodes, some kind of filter has to be inserted between the inverter and the grid to attenuate the switching harmonics. The filter is usually composed of inductors and capacitors, which allow the inverter to exchange active and reactive power with the grid by means of inverter control. The design guideline of the LCL-filter used here follows reference [1].

Filter capacitor C_f design To design C_f we have to consider reactive power variations due to the LCL-filter. The design base values can be defined as:

$$Z_b = \frac{V_{LL}^2}{P_n}, C_b = \frac{1}{\omega_g Z_b}, L_b = \frac{Z_b}{\omega_g},$$

where V_{LL}^2 is grid line-to-line RMS voltage, P_n is the rated active power, and $\omega_g = 2\pi f_g$ is the grid angular frequency. Filter capacitance is related to the base value C_b as a percentage of it. Setting the maximum power variation seen by the grid as 5% (empirical value 1% - 5%), we can obtain:

$$C_f = 0.05C_b$$

Filter inductors L_c and L_g design At low frequencies the LCL-filter behaves like an inductor with the total inductance of:

$$L_{dc} = L_c + L_g$$

Note that the current through filter capacitors C_f is negligible compared to that of the filter inductors. There is a relation between L_c and L_g that minimizes the voltage drop at the fundamental frequency and maximizes filtering ability. If we express L_c and L_g as a percentage of L_{dc} with $\alpha \in [0, 1]$, then:

$$L_c = \alpha L_{dc}, L_g = (1 - \alpha)L_{dc}$$

Since the LCL resonant circuit consists of L_c , C_f , and L_g all in parallel, the LCL resonant frequency is:

$$\omega_r = \sqrt{\frac{L_c + L_g}{L_c C_f L_g}}$$

Therefore the equivalent inductance L_{eq} that sets the resonant frequency can be defined as L_c and L_g in parallel:

$$L_{eq} = \frac{L_c L_g}{L_c + L_g} = \alpha(1 - \alpha)L_{dc}$$

The minimum L_{eq} is achieved when $L_c = L_g = 0.5L_{dc}$. By choosing L_{dc} to be 10% (empirical value) of the base value L_b , L_c and L_g are easily determined:

$$L_c = L_g = 0.05L_b$$

Active damping technique using filter capacitor currents

To suppress the high peak gain at the LCL resonant frequency, a damping resistor for the input filter can be placed as a passive damping method [2]. Passive damping is a simple approach but introduces additional losses, while active damping solves the problem through a control modification with a virtual resistor which is lossless.

Fig. 4 depicts the single-phase equivalent ideal LCL-filter and its corresponding block diagram [1]. Fig. 5 demonstrates the case of a damped filter, where the damping resistor is placed in series with the filter capacitor [1]. The block diagram in Fig. 5 shows that with a virtual gain component (emulating “RD” in Fig. 5) the same damping effect can be added to the control scheme of an ideal LCL-filter while removing the power losses of the physical damping resistor. For the active damping approach, filter capacitor currents have to be measured, which requires three (or only two for the case of balanced three-phase currents) additional analog in-/outputs. The filter in Fig. 4 can be described with

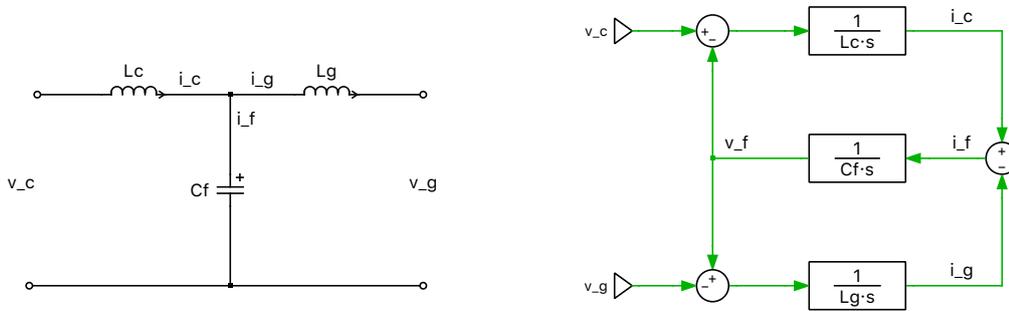


Figure 4: Single-phase equivalent ideal LCL-filter and corresponding block diagram

the state equations in the s -domain:

$$v_c(s) = sL_c i_c(s) + v_f(s)$$

$$v_g(s) = v_f(s) - sL_g i_g(s)$$

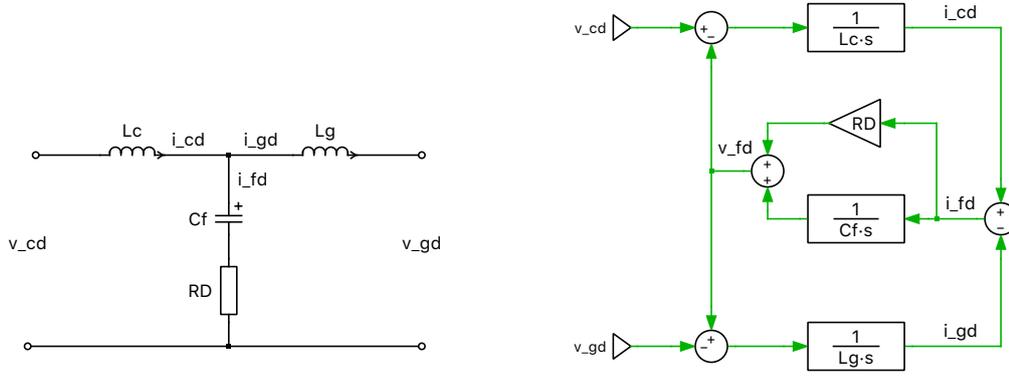


Figure 5: Single-phase equivalent damped LCL-filter and model, damping resistor in series with capacitor

$$v_f(s) = \frac{i_f(s)}{sC_f}$$

$$i_c(s) = i_f(s) + i_g(s)$$

The voltage and current transfer functions of the ideal LCL-filter are therefore:

$$H_{v_f}(s) = \frac{v_f(s)}{v_c(s)} = \frac{1}{L_c C_f} \frac{1}{s^2 + \omega_r^2}$$

$$H_{i_f}(s) = \frac{i_f(s)}{v_c(s)} = \frac{i_f(s)}{v_f(s)} \frac{v_f(s)}{v_c(s)} = \frac{1}{L_c} \frac{s}{s^2 + \omega_r^2}$$

where ω_r is the resonant frequency defined before.

For the LCL-filter with damping resistance in Fig. 5 we have:

$$v_c^d(s) = s \cdot L_c \cdot i_c^d(s) + v_f^d(s)$$

$$v_g^d(s) = v_f^d(s) - s \cdot L_g \cdot i_g^d(s)$$

$$v_f^d(s) = i_f^d(s) \left(R_D + \frac{1}{sC_f} \right)$$

$$i_c^d(s) = i_f^d(s) + i_g^d(s)$$

The damping resistor R_D is often selected as one third of the impedance of the filter capacitor C_f at resonant frequency [1]:

$$R_D = \frac{1}{3\omega_r C_f}$$

Therefore we can derive the same voltage and current transfer functions of interest:

$$H_{v_f}^d(s) = \frac{v_f^d(s)}{v_c^d(s)} = \frac{1}{L_c C_f} \frac{1 + sR_D C_f}{s^2 + \omega_r^2(1 + sR_D C_f)}$$

$$H_{i_f}^d(s) = \frac{i_f^d(s)}{v_c^d(s)} = \frac{i_f^d(s)}{v_f^d(s)} \frac{v_f^d(s)}{v_c^d(s)} = \frac{1}{L_c} \frac{s}{s^2 + \omega_r^2(1 + sR_D C_f)}$$

For the case without damping resistance, we define:

$$H_{v_f}(s) = \frac{v_f(s)}{v_c(s)} = \frac{L_g}{s^2 L_c C_f L_g + L_c + L_g} = H_1(s)$$

$$\frac{i_f(s)}{v_f(s)} = sC_f = H_2(s)$$

For the case with damping resistance, we define:

$$H_{v_f}^d(s) = \frac{v_f^d(s)}{v_c^d(s)} = \frac{L_g(1 + sR_D C_f)}{s^2 L_c C_f L_g + (L_c + L_g)(1 + sR_D C_f)} = H_3(s)$$

For the active damping technique, we would like to achieve $H_3(s)$ without a physical R_D , but rather with a virtual resistor with the value of R_D . Fig. 6 shows the block diagram of the active damping control loop with the gain of K_{AD} . We want the closed-loop transfer function in Fig. 6 to be similar to $H_3(s)$.

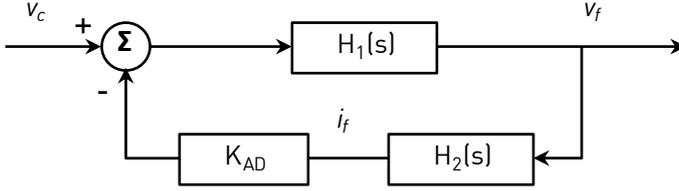


Figure 6: Active damping control loop block diagram with capacitor voltage/current as feedback

Thus in Fig. 6,

$$H_{CL}(s) = \frac{H_1(s)}{1 + H_1(s)H_2(s)K_{AD}} = \frac{\frac{L_g}{s^2 L_c C_f L_g + L_c + L_g}}{1 + \frac{L_g}{s^2 L_c C_f L_g + L_c + L_g} s C_f K_{AD}} = \frac{L_g}{s^2 L_c C_f L_g + L_c + L_g + s L_g C_f K_{AD}}$$

And with K_{AD} selected as:

$$K_{AD} = \frac{L_c + L_g}{L_g} R_D$$

we have

$$H_{CL}(s) = \frac{L_g}{s^2 L_c C_f L_g + L_c + L_g + s L_g C_f \frac{L_c + L_g}{L_g} R_D} = \frac{L_g}{s^2 L_c C_f L_g + (L_c + L_g)(1 + s R_D C_f)}$$

This final $H_{CL}(s)$ is close enough to $H_3(s)$ that we can neglect the term “ $R_D C_f$ ” in the numerator of $H_3(s)$ since it is much smaller than 1. Note that the implementation should be considered for both axis regulator for i_d and i_q . This virtual damping gain K_{AD} is located inside the controller subsystem (see later Fig. 7) as the Gain block “Virtual damping resistor”.

2.2 Three-Level Space-Vector Pulse-Width Modulation Scheme and Controls

The controller subsystem including measurement transformation, three-level SVPWM and closed-loop dq current controller are captured in Fig. 7. It contains Analog In and PWM Out blocks from the RT Box Target Support library. A generic description of these blocks is given in the RT Box Target Support package documentation or the “Boost Converter” RT Box demo model.

The i_d and i_q current controllers are designed using the Magnitude Optimum Criterion based on the following transfer function:

$$H_{OL}(s) \approx \frac{1}{R_g + R_c + (L_g + L_c)s}$$

This neglects the small current flowing into the filter capacitors and the stiff grid inductance $L_{grid} \ll L_g$.

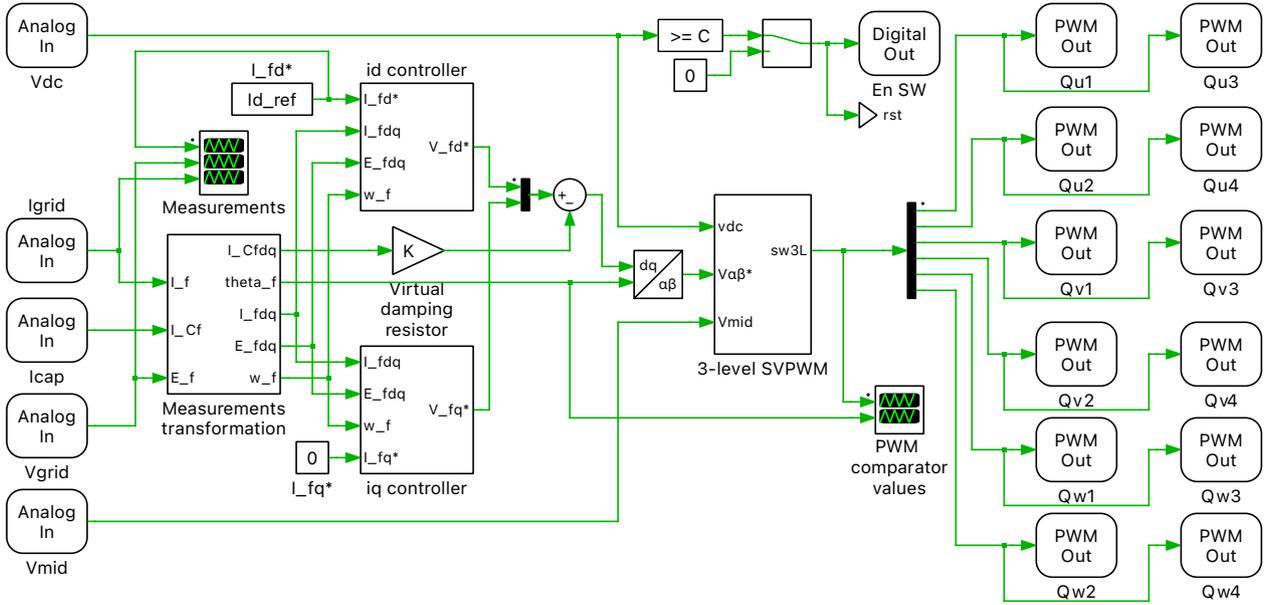


Figure 7: Control scheme of the grid-connected three-level NPC inverter using SVPWM method

SVPWM Scheme

There are three NPC legs (phases u, v, and w) shown in Fig. 3. Each leg contains four switches Q_{x1} , Q_{x2} , Q_{x3} , and Q_{x4} ($x = u, v, \text{ and } w$), and these four switches must be controlled in two complementary pairs. Q_{x1} and Q_{x3} make one complementary pair, while Q_{x2} and Q_{x4} make the other pair. By controlling these four switches the inverter output allows for three different voltage levels. Table 1 lists the three valid states for each leg, in which P means a switch leg is connected to the positive DC rail, N means it is connected to the negative DC rail, and O means it is connected to the neutral-point potential.

Table 1: Output status of each leg based on different switching combination of Q_{x1} - Q_{x4}

Switch No.	Q_{x1}	Q_{x2}	Q_{x3}	Q_{x4}	Phase voltage	Leg status
1	ON	ON	OFF	OFF	$\frac{V_{dc}}{2}$	P
2	OFF	OFF	ON	ON	$-\frac{V_{dc}}{2}$	N
3	OFF	ON	ON	OFF	0	O

Thus, in total there are 27 states of the three-level VSI which can be mapped to the space-vector diagram, depicted in Fig. 8. Assuming a reference vector V_{ref} , according to the theory of SVPWM, we need to find the two nearest vectors V_X , V_Y and one zero vector V_Z in order to synthesize V_{ref} . Therefore, vector PNN (V_X), PON (V_Y) and NNN (V_Z) in Fig. 8 can be selected accordingly to form V_{ref} .

If the dwelling time of vector V_X , V_Y and V_Z inside a switching period T_{sw} are T_X , T_Y and T_Z respectively, the following functions must be satisfied:

$$V_X T_X + V_Y T_Y + V_Z T_Z = V_{ref} T_{sw} \quad (1)$$

$$T_X + T_Y + T_Z = T_{sw} \quad (2)$$

However, it is difficult to determine V_X , V_Y and V_Z by the angle only, which is used in the 2-level SVPWM scheme, because the reference vector can be located in different sectors even if the angle is

as the mapping vector $V_{\text{map}1} = V_0$. After the mapping we can get the hexagon shown in Fig. 10, which is the same vector diagram as the 2-level SVPWM.

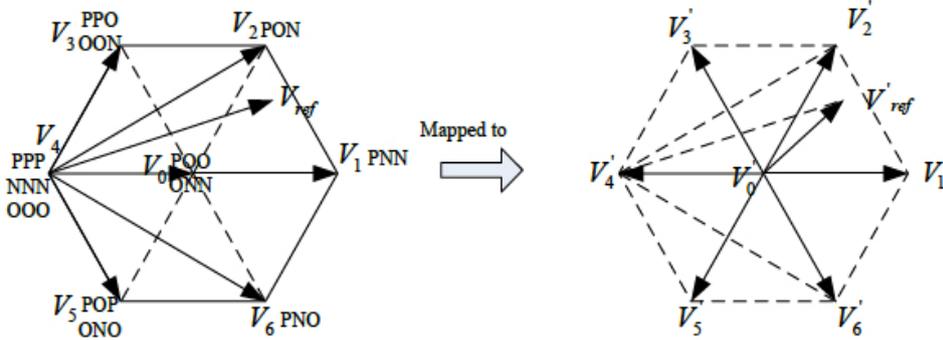


Figure 10: Mapping from the 3-level SVPWM to a 2-level SVPWM in sub-hexagon 1

From Fig. 10, it can be seen that V'_{ref} is still in the mapped sub-hexagon 1, and we can easily determine that the dwelling vectors are V'_1 and V'_2 . The V'_0 can be taken as the zero vector in the 2-level SVPWM. So, we can get the following function:

$$V'_1 T_X + V'_2 T_Y + V'_0 T_Z = V'_{\text{ref}} T_{\text{sw}} \quad (4)$$

Note that Eq. (2) is still valid here. Combing Eq. (2) and Eq. (4), one can derive:

$$(V_1 - V_{\text{map}1}) T_X + (V_2 - V_{\text{map}1}) T_Y + (V_0 - V_{\text{map}1}) T_Z = (V_{\text{ref}} - V_{\text{map}1}) T_{\text{sw}} \quad (5)$$

which means:

$$V_1 T_X + V_2 T_Y + V_0 T_Z = V_{\text{ref}} T_{\text{sw}} \quad (6)$$

Thus, if the dwelling time of V'_1 , V'_2 , and V'_0 can be calculated, the original vector dwelling time can be determined. From the mapping in Fig. 10, the vector selection and the dwelling time calculation of the 3-level SVPWM are converted to 2-level SVPWM totally.

Different main sectors have different mapping vectors. Table 2 summarizes the mapping vector for each main sector.

Table 2: Mapping vector for each main sector

Main sector No.	Mapping vector	Element of α	Element of β
1	POO or ONN	$\frac{V_{\text{dc}}}{3}$	0
2	PPO or OON	$\frac{V_{\text{dc}}}{6}$	$\frac{\sqrt{3}V_{\text{dc}}}{6}$
3	OPO or NON	$-\frac{V_{\text{dc}}}{6}$	$\frac{\sqrt{3}V_{\text{dc}}}{6}$
4	OPP or NOO	$-\frac{V_{\text{dc}}}{3}$	0
5	OOP or NNO	$-\frac{V_{\text{dc}}}{6}$	$-\frac{\sqrt{3}V_{\text{dc}}}{6}$
6	POP or ONO	$\frac{V_{\text{dc}}}{6}$	$-\frac{\sqrt{3}V_{\text{dc}}}{6}$

The main sector number can be defined by the angle of the V_{ref} in the α - β coordinate plane. For example, according to Fig. 9, the angle range of main sector 1 is $[-\frac{\pi}{3}, \frac{\pi}{3}]$, and the angle range of main sector 2 is $[0, \frac{2\pi}{3}]$. Thus, the overlapped area between main sector 1 and 2 can be split into the two adjacent areas equally, in order to have monopolized angle area for each sector. Fig. 11 depicts the simplified definition of the six main sectors.

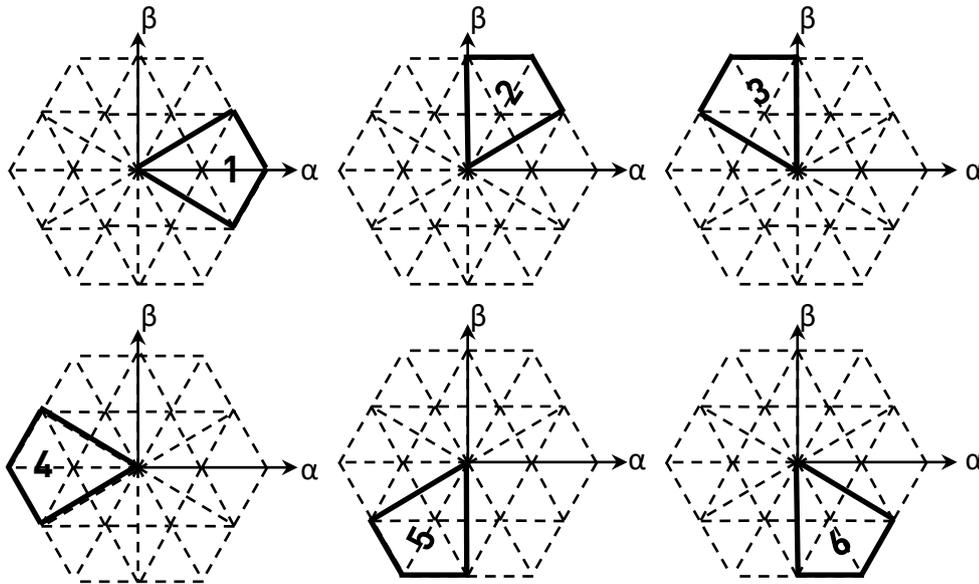


Figure 11: Simplified definition of the six main sectors

In the 2-level SVPWM, the first step is to find the sector number which can determine the dwelling vectors. The second step is to calculate the dwelling time for each of the selected vectors. According to the principle of 3-level SVPWM, when the main sector is determined and all the vectors are mapped to the main sector, the same process done in 2-level SVPWM can be implemented to determine the sub-sector and calculate the dwelling times for each dwelling vectors. Here in this demo model, a simple and effective way is deployed [3] to calculate the duty cycle for each switching pair out of the dwelling time of each dwelling vector.

Again we take main sector 1 as an example. According to Fig. 9 there is no N status for u phase. Besides, if OON, ONO, and OOO are selected for the vector mapping, there will be no P status for the v and w phases. For the u phase, we represent the P status with 1, and the O status with 0. For v and w phases, we represent the O status with 1, and the N status with 0. Fig. 12 depicts this replacement operation. After this downsizing operation, the dwelling time for three vectors can be determined. As shown in Fig. 12, T_X is the dwelling time of status 100, T_Y represents the one of status 110, and T_Z is the time for status 111 and 000.

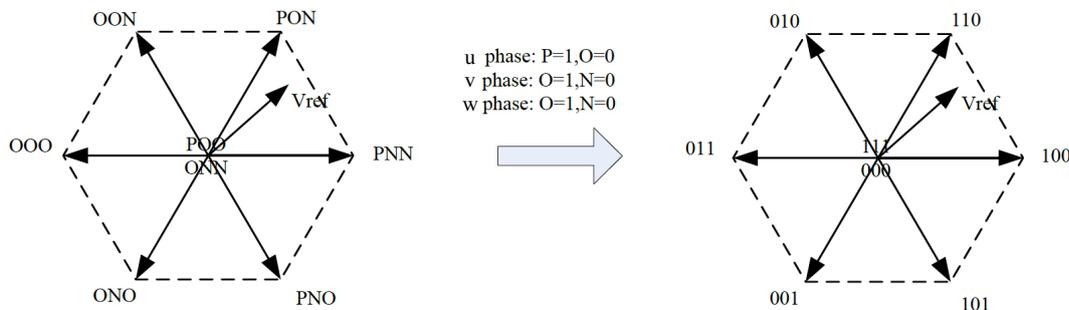


Figure 12: The status replacement rule downsizing 3-level vector diagram to 2-level one in main sector 1

Here we can calculate the three duty cycles for the upper switches out of the three complementary switch pairs (d_1 , d_2 , and d_3), with the symmetrical PWM mode. The left side of Fig. 13 shows that effectively, the resulting 2-level vector sequence is 000 - 100 - 110 - 111 - 110 - 100 - 000. Next, if we apply the same status replacement rule as in Fig. 12, we get the right part of Fig. 13. Thus we can

achieve the 3-level vector sequence: ONN - PNN - PON - POO - PON - PNN - ONN.

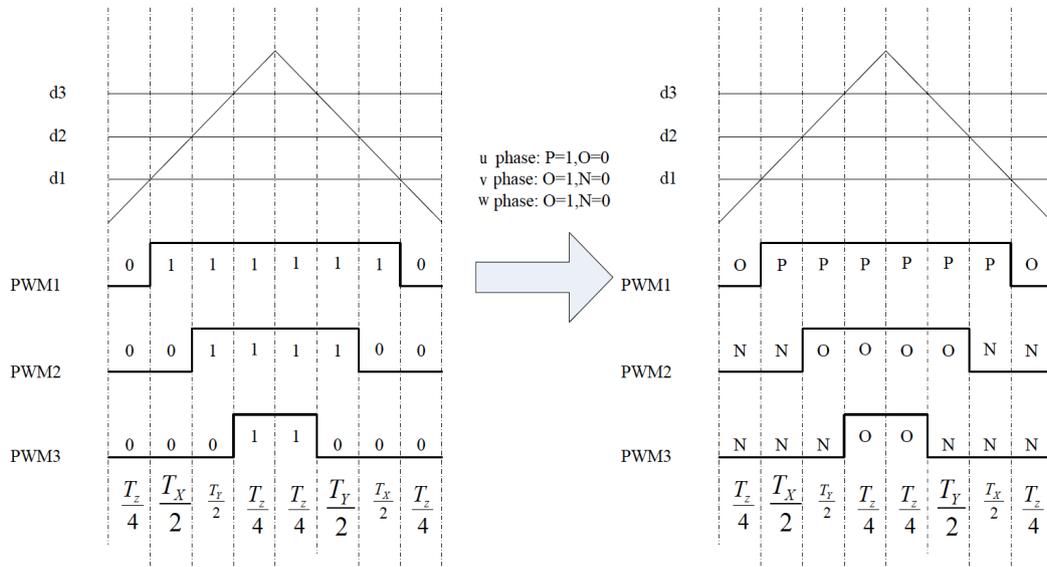


Figure 13: Symmetrical 2-level SVPWM applying the status replacement rule back to a 3-level SVPWM

Table 3 summarizes this status replacement rule for each main sector. The positive pair of power switches is Q_{x1} and Q_{x3} ($x = u, v, w$); the negative pair of the power switches is Q_{x2} and Q_{x4} ($x = u, v, w$). We also define the same status 0 and 1 for each pair as the 2-level SVPWM. So for the main sector 1, since in one switching cycle, u phase has no N status, the negative pair u phase is always 0. Similarly for the v and w phases, since they have no P status, the positive pair is always 0. That means in the main sector 1, d1 can be assigned to the positive pair of u phase (i.e. Q_{u1} has duty cycle of d1, and Q_{u3} has complementary logic to Q_{u1}), d2 can be assigned to the negative pair of v phase (i.e. Q_{v2} has duty cycle of d2, and Q_{v4} has complementary logic to Q_{v2}), and d3 can be assigned to the negative pair of w phase (i.e. Q_{w2} has duty cycle of d3, and Q_{w4} has complementary logic to Q_{w2}). The process can be extended to all the six main sectors and Table 4 shows this duty cycle assignment rule.

Table 3: Status replacement rule for each main sector

Main sector No.	U phase		V phase		W phase	
	1	0	1	0	1	0
1	P	O	O	N	O	N
2	P	O	P	O	O	N
3	O	N	P	O	O	N
4	O	N	P	O	P	O
5	O	N	O	N	P	O
6	P	O	O	N	P	O

The simplified 3-level SVPWM algorithm discussed above is implemented using the C-Script block and the output provides six modulation index values for Q_{u1} , Q_{u2} , Q_{v1} , Q_{v2} , Q_{w1} and Q_{w2} individually, as summarized in Table 4. The complementary signal for each of them is realized by configuring the opposite Polarity in the corresponding PWM Out blocks.

Table 4: Duty cycle assignment rule for each main sector

Main sector No.	U phase		V phase		W phase	
	Positive pair (Qu1)	Negative pair (Qu2)	Positive pair (Qv1)	Negative pair (Qv2)	Positive pair (Qw1)	Negative pair (Qw2)
1	d1	1	0	d2	0	d3
2	d1	1	d2	1	0	d3
3	0	d1	d2	1	0	d3
4	0	d1	d2	1	d3	1
5	0	d1	0	d2	d3	1
6	d1	1	0	d2	d3	1

Neutral-point balancing technique

The active neutral-point balancing technique implemented in this demo model is based on [4]. Neutral-point current i_{NP} is denoted as the current coming out of the DC neutral point shown in Fig. 3. According to the SVPWM vector diagram shown in Fig. 8, Table 5 summarizes all the vectors that influence the neutral-point balance. $i_{u,v,w}$ denotes the current direction going out of the switching node of the three-level phase leg entering the grid side.

Small vectors come in pairs, e.g. POO and ONN, and they disturb the neutral point with exactly the same current value, but just the opposite sign. Furthermore, as shown in Fig. 12, POO and ONN are the new zero vectors in the downsized 2-level vector diagram in main sector 1. Therefore, the active control of neutral-point voltage lies in the manipulation of this new zero vector pair. This requires measuring the middle-point voltage (v_{mid} in Fig. 3) in addition to the full DC voltage (v_{dc} in Fig. 3). As a result, the total zero vector dwelling time T_Z in Fig. 13 will be split between its 2-level “111” and “000” vectors, each proportional to its half DC voltage. Since the medium vectors disturb the neutral point and there is no vector that can be used to balance with the medium vector inside each main sector, some neutral-point variation can still be observed on the scale of each main sector. For more details and limitations of this method, please refer to [4].

Table 5: Neutral-point current i_{NP} for different space vectors

Positive Small Vectors	i_{NP}	Negative Small Vectors	i_{NP}	Medium Vectors	i_{NP}
ONN	i_u	POO	$-i_u$	PON	i_v
PPO	i_w	OON	$-i_w$	OPN	i_u
NON	i_v	OPO	$-i_v$	NPO	i_w
OPP	i_u	NOO	$-i_u$	NOP	i_v
NNO	i_w	OOP	$-i_w$	ONP	i_u
POP	i_v	ONO	$-i_v$	PNO	i_w

3 Simulation

This model can run both, in offline mode on a computer or in real-time mode on the PLECS RT Box. For the real-time operation, two RT Boxes (referred to as “Plant” and “Controller”) need to be set up as demonstrated in Fig. 14.


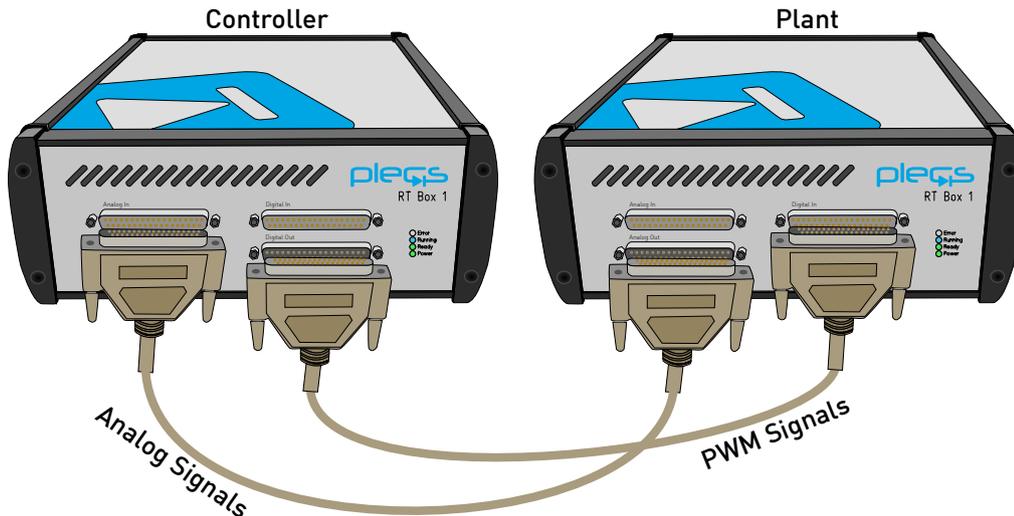


Figure 14: Interconnection of the two RT Boxes running the plant and controller models

Please follow the instructions below to run a real-time model on two RT Boxes:

- Connect the Analog Out interface of the “Plant” RT Box to the Analog In interface of the “Controller” RT Box, and the Digital In interface of the “Plant” RT Box to the Digital Out interface of the “Controller” RT Box (e.g. using two DB37 cables shown in Fig. 14).
- From the **System** tab of the **Coder options...** window, select the “Plant” and **Build** it onto the “Plant” RT Box. Then, select “Controller” and **Build** it onto the “Controller” RT Box.
- Once the models are uploaded, from the **External Mode** tab of the **Coder options...** window, **Connect** to both RT Boxes and **Activate autotriggering**.

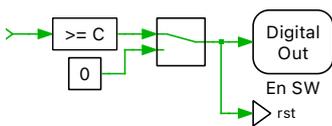Note As shown below, during runtime the Manual Signal Switch before the Digital Out named “En SW” on the “Controller” subsystem in its default Up position enables switching. Change it to the Down position disables switching and also resets the id-iq PI Controller integral part.



Key waveforms can be observed in the “Measurements” Scopes individually placed in the “Plant” and “Controller” subsystems. Since the neutral-point balancing technique is implemented in the controller, the middle-point DC voltage can be controlled at around 400 V operating at steady state even though the initial voltages on the upper and lower DC capacitors are 450 V and 350 V, respectively. A DC voltage step change can be applied on the “Sun” Constant block, such as from 1 to 1.2. This implies a sun radiation change on the PV panels. Fig. 15 captures the response to such an event on the “Plant” side. One can see that the middle-point DC voltage rises from 400 V to 480 V, and stabilizes afterwards. Accordingly, grid currents are controlled to deliver the same d-q axis currents after short dynamics.

Next, keeping the DC voltage at the default value of 800 V, on the controller side of the “Virtual damping resistor”, the Gain block can be changed to 80 % of the original value $((L_c + L_g)/L_g * R_D)$. A moderate amount of ringing in current waveforms can be observed due to inadequate damping. This is demonstrated in Fig. 16. Changing the “Virtual damping resistor” gain back to the original value, this unwanted ringing can be eliminated.

In the end, since PI controllers are designed individually for d-q axis currents, a d-axis current reference step-down is performed by changing the “ I_{fd}^* ” Constant block, such as to 80 % of its original

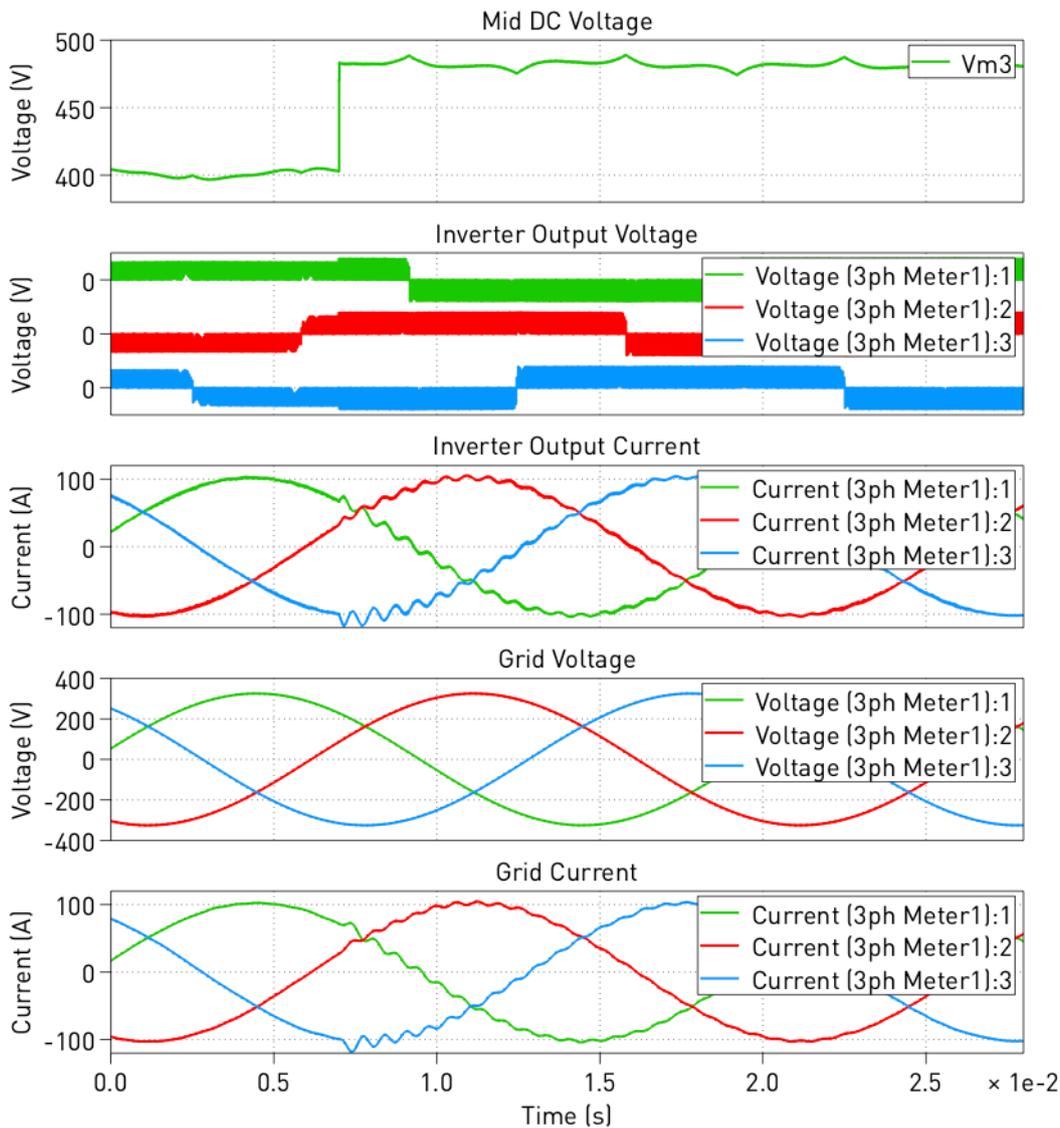


Figure 15: Plant box side real-time simulation result for inverter under DC voltage rise

value. Fig. 17 captures this reference step. The grid currents are controlled to the new d-axis reference value, while maintaining a power factor of 1 due to the unchanged q-axis current reference of 0.

4 Conclusion

This RT Box demo model demonstrates a three-level grid-connected NPC inverter under closed-loop control with d-q axis continuous PI current controllers. The demo model can run in both offline simulation and real-time operation for hardware-in-the-loop tests or rapid control prototyping. The controller subsystem runs on one RT Box with a discretization step size of $50 \mu\text{s}$, which is the size of the switching period, and the plant subsystem runs with a discretization step size of $7 \mu\text{s}$ on a second RT Box. The actual execution time of the controller model is around $2.7 \mu\text{s}$, while the plant model runs in $6.7 \mu\text{s}$ on the other RT Box.

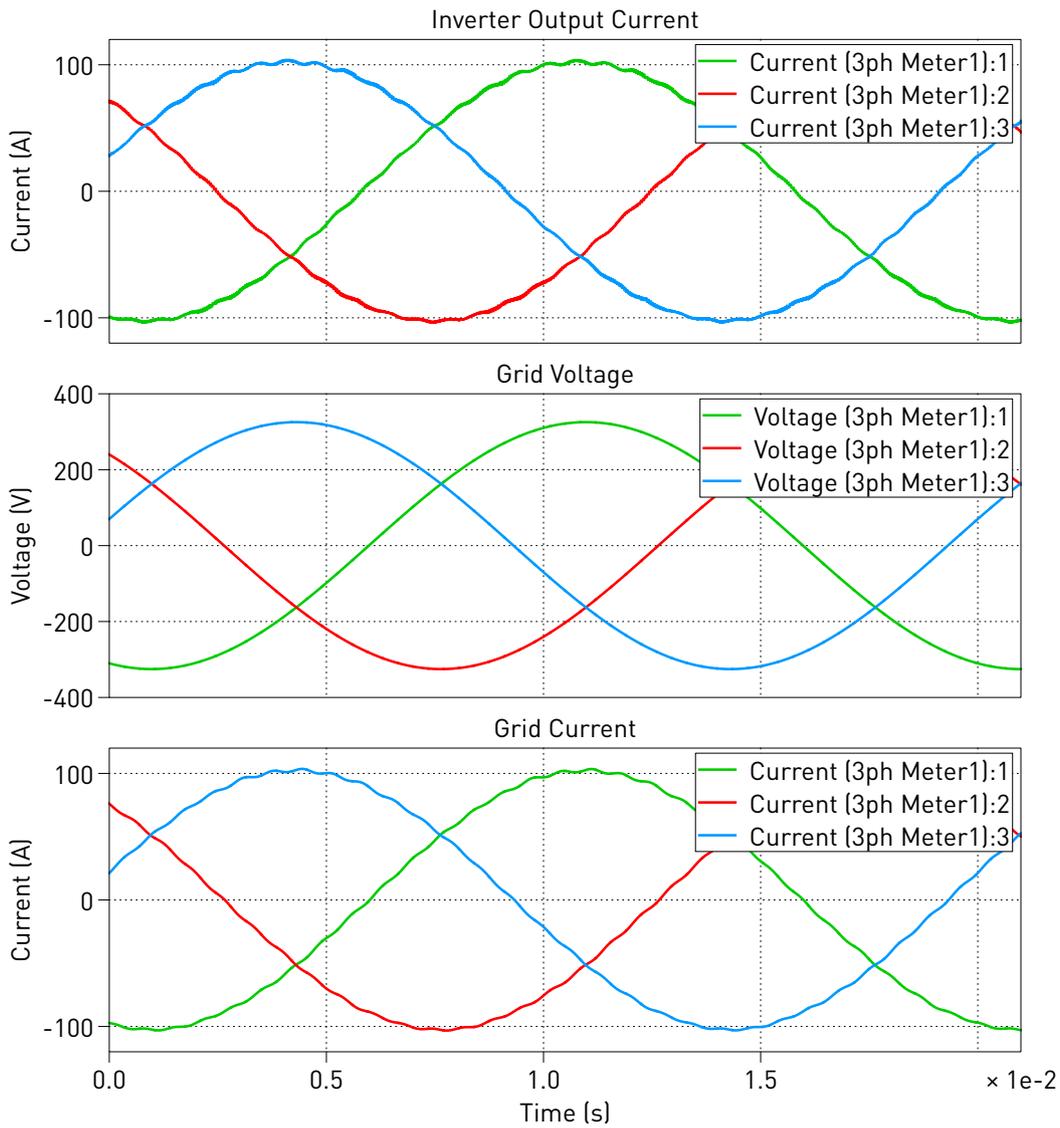


Figure 16: Plant box side real-time simulation result for inverter with poorly damped virtual resistor

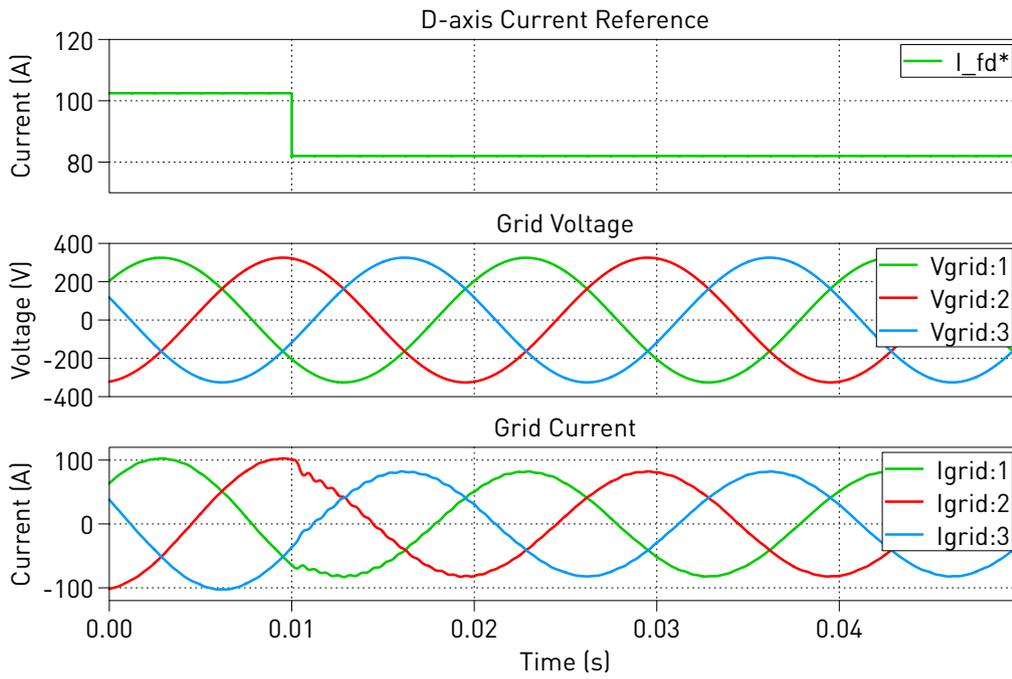


Figure 17: Controller box side real-time simulation result for inverter under d-axis current reference step

References

- [1] R. Teodorescu, M. Liserre and P. Rodriguez, “Grid converters for photovoltaic and wind power systems”, pp. 289-311, IEEE, Wiley, 2011.
- [2] R. W. Erickson, “Optimal single resistors damping of input filters”, *APEC '99, Fourteenth Annual Applied Power Electronics Conference and Exposition*, vol.2, pp. 1073-1079, March 1999.
- [3] V. Xue, “Center-Aligned SVPWM Realization for 3-Phase 3-Level Inverter (Application Report)”, Texas Instruments, October 2012.
- [4] N. Celanovic and D. Boroyevich, “A comprehensive study of neutral-point voltage balancing problem in three-level neutral-point-clamped voltage source PWM inverters”, *IEEE Transactions on Power Electronics*, vol. 15, no. 2, pp. 242-249, March 2000.

Revision History:

RT Box Target Support Package 1.8.3
RT Box Target Support Package 2.1.7

First release
Add the enable/disable switching
scheme and use the PI Controller
component from the library

How to Contact Plexim:

☎	+41 44 533 51 00	Phone
	+41 44 533 51 01	Fax
✉	Plexim GmbH Technoparkstrasse 1 8005 Zurich Switzerland	Mail
@	info@plexim.com	Email
	http://www.plexim.com	Web

RT Box Demo Model

© 2002–2022 by Plexim GmbH

The software PLECS described in this document is furnished under a license agreement. The software may be used or copied only under the terms of the license agreement. No part of this manual may be photocopied or reproduced in any form without prior written consent from Plexim GmbH.

PLECS is a registered trademark of Plexim GmbH. MATLAB, Simulink and Simulink Coder are registered trademarks of The MathWorks, Inc. Other product or brand names are trademarks or registered trademarks of their respective holders.